

Alireza Javadi, Guy Olivier, Frédéric Sirois, and André Youmssi

Electrical Engineering Department École Polytechnique de Montréal, Canada

The 9th International Conference on Environment and Electrical Engineering (EEEIC)

Prague, Czech Republic, May 16 - 19, 2010





Summary:



- ✓ Introduction
- ✓ Instantaneous active and reactive powers theory
- ✓ Equipments used for the laboratory tests
- ✓ Real-time results of the power hardware in the loop (PHIL)
- √ Conclusion



Introduction:



- Proliferation of power electronics converters and electronic equipments has dramatically increased electric pollution in electrical distribution power systems.
 - ✓ Active filters (capable of injecting distorted currents in order to cancel harmonics coming from non-linear loads)
- Consequently, many theories have been developed to control active filters.
 - ✓ Instantaneous power (*p-q theory*), an overview of the instantaneous compensation theory will be presented.
- To illustrate the effectiveness of such compensation an HIL system is realized in laboratory.
 - ✓ PHIL system with a real-time Opal-RT simulator.
- The analysis of the real-time results to proven the instantaneous compensation of the controller.







$$v = \begin{bmatrix} v_{an} \\ v_{bn} \\ v_{cn} \end{bmatrix} \quad , i = \begin{bmatrix} i_a \\ i_b \\ i_c \end{bmatrix}$$

$$i_{\alpha\beta 0} = \begin{bmatrix} i_{\alpha} \\ i_{\beta} \\ i_{0} \end{bmatrix} = \underbrace{\sqrt{\frac{2}{3}}} \begin{bmatrix} 1 & -\frac{1}{2} & -\frac{1}{2} \\ 0 & \sqrt{3}/2 & -\frac{\sqrt{3}}{2} \\ \frac{1}{\sqrt{2}} & \frac{1}{\sqrt{2}} & \frac{1}{\sqrt{2}} \end{bmatrix} \times \begin{bmatrix} i_{a} \\ i_{b} \\ i_{c} \end{bmatrix}$$

$$p_{3\varphi} = \vec{v} \cdot \vec{i} = v_{an}i_a + v_{bn}i_b + v_{cn}i_c$$
$$= v_{\alpha}i_{\alpha} + v_{\beta}i_{\beta} + v_{0}i_{0} = p + p_{0}$$

$$\vec{q} \triangleq \vec{v} \times \vec{i} \qquad q = v_{\beta} i_{\alpha} - v_{\alpha} i_{\beta}$$

Instantaneous powers are divided into an average value and an oscillating portion:

$$p=ar{p}+ ilde{p}$$

$$p_0=ar{p}_0+ ilde{p}_0$$

$$q=ar{q}+ ilde{q}$$


Where "·" is the internal product of vectors and "×" denotes the exterior product of vectors




Equipments:





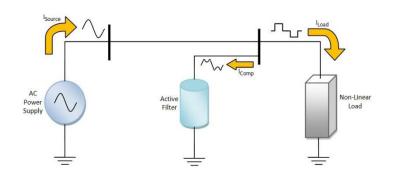

Non-linear load

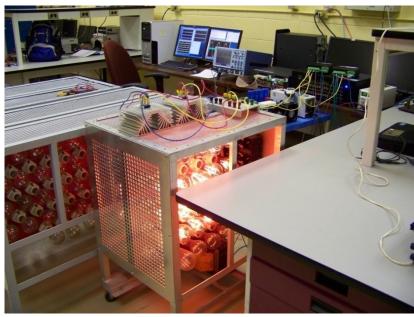




Equipments:





Real-time Simulator
Probes
Patch panel
Three phase power Inverter

RT-Lab Interface

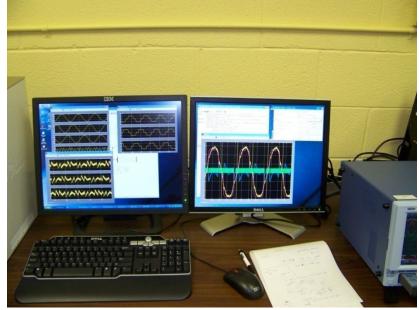








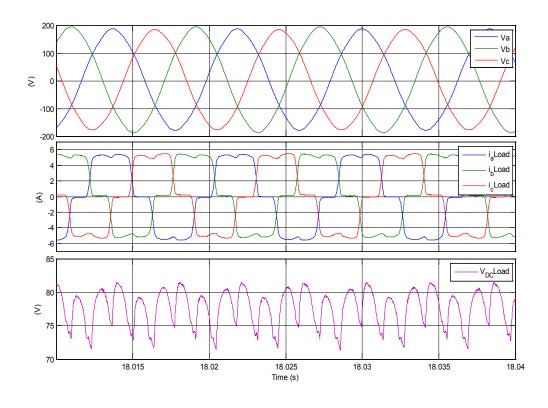Instantaneous non-active power compensation Instantaneous voltages and currents:












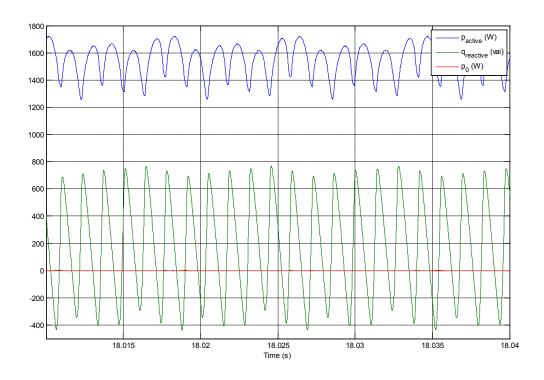Instantaneous non-active power compensation
Instantaneous active, reactive, and zero-sequence powers:












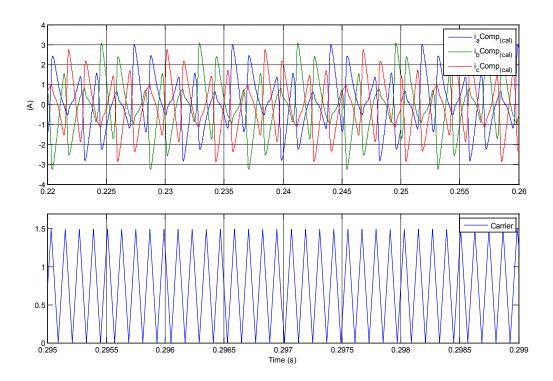Instantaneous non-active power compensation
Instantaneous calculated compensating currents, carrier (8.33 kHz):












Instantaneous non-active power compensation

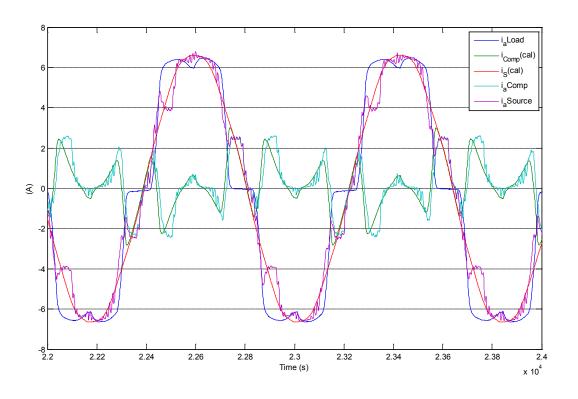Instantaneous load, source, compensating, and calculated currents:








Real-time results of the PHIL:



Instantaneous non-active power compensation

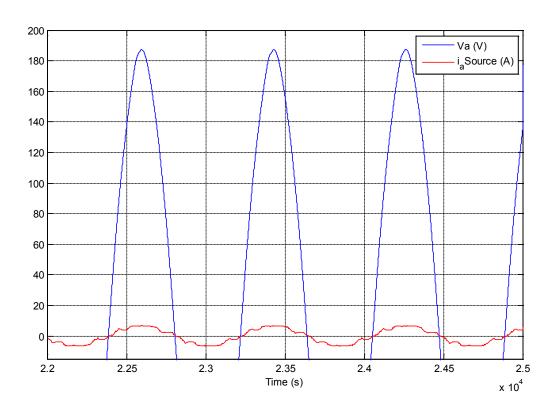First phase ("a") source voltage and current after compensation:







Conclusion:



- ✓ This paper describes active filters built around a commercial inverter.
- ✓ The Opal-RT real-time simulator was used to implement a real-time controller based on the p-q theory to have a powers Hardware in the loop system (PHIL).
- ✓ Data were acquisitioned instantaneously and results were analyzed.
- ✓ Despite the use of a PWM in this paper, currents produced by the inverter have had exactly the same shape as the calculated compensating currents.
- ✓ By means of the real-time test, the powerfulness of active filters based on the instantaneous theory was illustrated, as well as the capabilities of the real-time simulator was demonstrated.





Thank you ruguk hon



